

ECE 351 - 52

SIGNALS AND SYSTEMS 1

LAB 4

*Submitted By :*  
Owen Blair

# Contents

1	Important Notes . . . . .	2
2	Part 1 Deliverables . . . . .	2
3	Part 2 Deliverables . . . . .	2
4	Equations . . . . .	3
5	Results . . . . .	3
6	Listings . . . . .	5
7	Questions . . . . .	7
	7.1 Question 1 . . . . .	7

## 1 Important Notes

It is important to note that `plt.show()` is needed at the end of the python code to properly show the plots of each function. It was not included in every section of code that plots a function(s) because it is assumed that its included at the end the code.

The web address to the GitHub where  $\text{\LaTeX}$  code is stored is here:  
[https://github.com/Blairis123/ECE351\\_Reports](https://github.com/Blairis123/ECE351_Reports)

The web address to the GitHub where the Python code is here:  
[https://github.com/Blairis123/ECE351\\_Code](https://github.com/Blairis123/ECE351_Code)

## 2 Part 1 Deliverables

The goal of part one is to plot the impulse response of the circuit in *Figure 1: Circuit*. This was done in two ways. One was a hand solved time domain response implemented as a function and the second is using `scipy.signal.impulse()` function with the s-domain transfer function of the circuit. The function that was found by hand can be found in *Listing 1: Hand Solved Function Using Python* and the plot of the hand solved impulse response compared to the `scipy.signal.impulse()` plot can be found in *Figure 2: Hand-Solved Vs signal.impulse()*.

## 3 Part 2 Deliverables

Part two is about comparing the step response of the circuit to the impulse response of the circuit. The step response is found by using the `scipy.signal.step()` function and compared to the impulse response found in Part 1. The code to generate and plot the `scipy.signal.step()` compared with the `scipy.signal.impulse()` can be found in *Listing 2: Step Response* and the plot in *Figure 3: Step Vs Impulse*. The equation for the final value theorem can be found in the *Equations Used* section of this report. A further discussion of the final value theorem can be found in the *Equations Used* section as well.

## 4 Equations

*Equation 1: Definition of the Final Value Theorem*

$$\lim_{t \rightarrow \infty} h(t) = \lim_{s \rightarrow 0} sH(s)$$

Given this we can then input the values of R, L, and C from *Figure 1*. This results in about:

$$\lim_{t \rightarrow \infty} \left( \frac{g}{\omega} * e^{-\frac{1}{2} * t} * \sin(\omega t + \angle g) \right) = \lim_{s \rightarrow 0} \left( \frac{10^4 * s}{s^2 * 10^4 * s + 3.7037 * 10^8} \right)$$

Knowing that  $g = -\frac{1}{2} * 18584j = 18584 \angle 90.002$  and  $\alpha = -\frac{1}{2}$  and is multiplied by t, it is safe to say that  $\lim_{t \rightarrow \infty} h(t) = 0$ . Regarding  $\lim_{s \rightarrow 0} sH(s)$  it can be seen that the numerator goes to zero and the denominator goes to  $\frac{1}{L * C}$  so  $sH(s)$  must also go to zero.

## 5 Results

*Figure 1: Circuit*

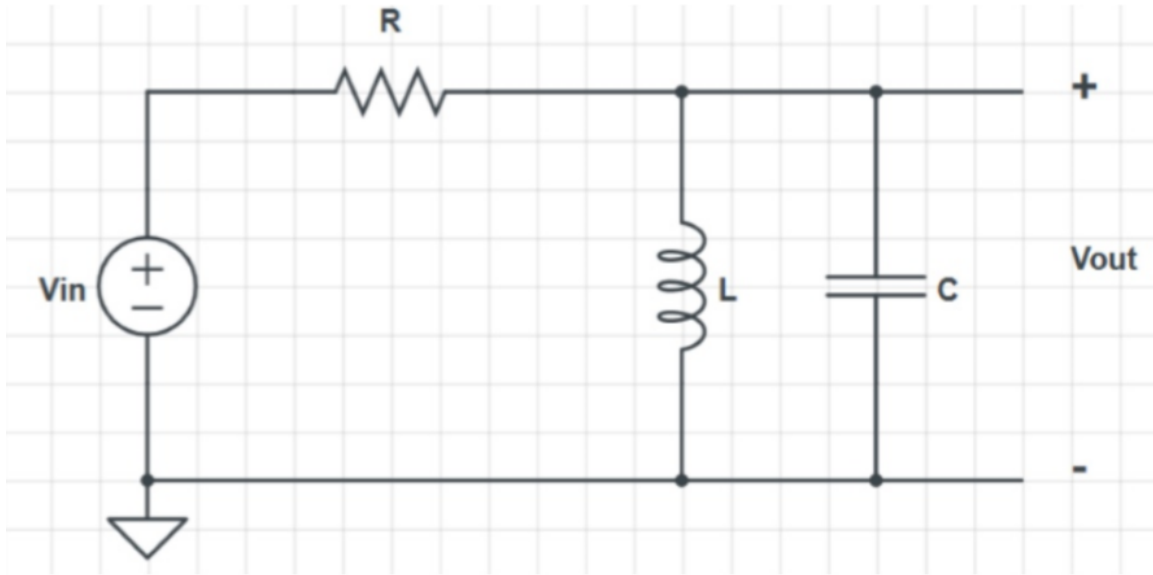


Figure 1:  $R = 1k\Omega$ ,  $L = 27 \text{ mH}$ ,  $C = 100 \text{ nF}$

Figure 2: Hand-Solved Vs `signal.impulse()`


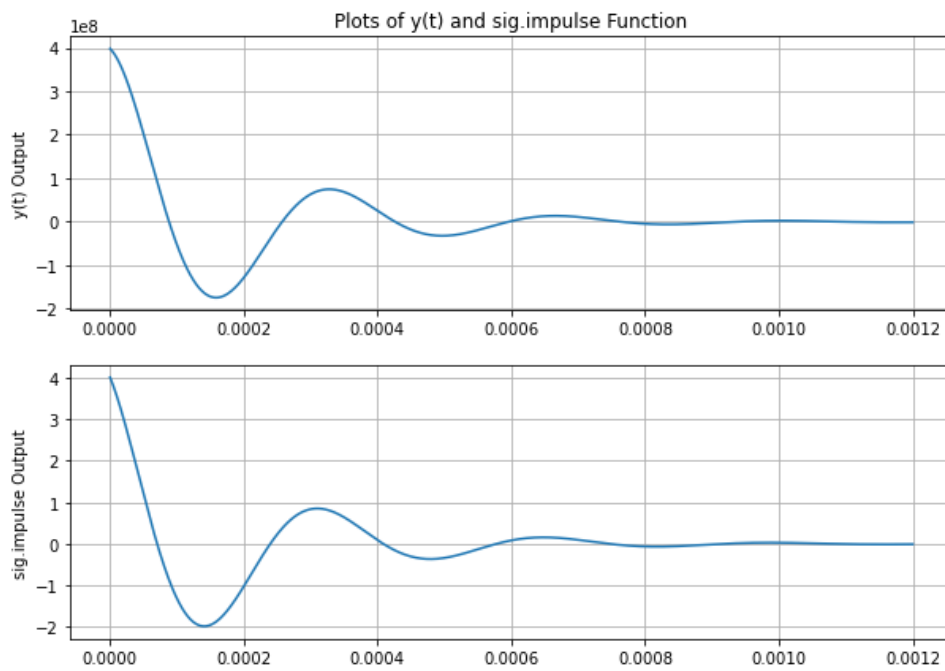


Figure 3: Step Vs Impulse

 

## 6 Listings

*Listing 1: Hand Solved Function Using Python*

```

1  #DEFINE FUNCTION TO USE FOR HAND SOLVED PLOT
2  def func2Plot(t, R, L, C):
3
4      X = (1/(R*C))
5      tmpX = -0.5 * ((1/(R*C))**2)
6      tmpY = 0.5 * X * (m.sqrt((X**2)) - (4/(L*C)))
7
8      magOfG = m.sqrt((tmpX**2) + (tmpY**2))
9
10     tmpTanX = 0.5 * (m.sqrt((X**2)) - (4/(L*C)))
11     tmpTanY = -0.5 * ((1/(R*C))**2)
12
13     degOfG = m.atan(tmpTanX / tmpTanY)
14
15     omega = 0.5 * np.sqrt(X**2 - 4*(1/np.sqrt(L*C))**2 + 0*1j)
16     alpha = (-0.5) * X
17
18     y = (magOfG/np.abs(omega)) * np.exp(alpha * t) * np.sin(np.abs(
19     omega) * t + degOfG) * stepFunc(t, 0, 1)
20
21     return y
22
23 #-----END FUNCTIONS-----#
24
25     #Make steps for t! From 0 to 1.2 ms this would be
26 steps = 1e-6
27
28     #t for part 1
29 start = 0
30 stop = 1.2e-3
31
32     #Define a range of t_pt1. Start @ 0 go to 20 (+a step) w/
33     #a stepsize of step
34 t = np.arange(start, stop + steps, steps)
35
36 #-----PT1-----
37
38     #For circuit-----R L C DEF-----
39 R = 1e3
40 L = 27e-3
41 C = 100e-9
42
43 y = func2Plot(t, R, L, C)
44
45 num = [0, 1/(R*C), 0] #Creates a matrix for the numerator
46 den = [1, 1/(R*C), (1/(L*C))] #Creates a matrix for the denominator

```

```

44
45 tout , ySig = sig.impulse ((num , den), T = t)
46
47 ySig = ySig * (4e-4)
48     #Make plots
49 plt.figure(figsize=(10,7))
50 plt.subplot(2,1,1)
51 plt.plot(t,y)
52 plt.grid()
53 plt.ylabel('y(t) Output')
54 plt.title('Plots of y(t) and sig.impulse Function')
55
56 plt.subplot(2,1,2)
57 plt.plot(t,ySig)
58 plt.grid()
59 plt.ylabel('sig.impulse Output')

```

*Listing 2: Step Response*

```

1     #For circuit-----RLC DEF-----
2 R = 1e3
3 L = 27e-3
4 C = 100e-9
5
6 y = func2Plot(t, R, L, C)
7
8 num = [0, 1/(R*C), 0] #Creates a matrix for the numerator
9 den = [1, 1/(R*C), (1/(L*C))] #Creates a matrix for the denominator
10
11 tout , ySig = sig.impulse ((num , den), T = t)
12
13 ySig = ySig * (4e-4)
14 #-----PT2 CODE-----
15 tout2 , yStep = sig.step ((num , den), T = t)
16
17 #-----PT 2 PLOTS-----
18 plt.figure(figsize=(10,7))
19 plt.subplot(2,1,1)
20 plt.plot(t,ySig)
21 plt.grid()
22 plt.ylabel('ySig Output')
23 plt.title('Plots of sig.impulse and sig.step Function')
24
25 plt.subplot(2,1,2)
26 plt.plot(t,yStep)
27 plt.grid()
28 plt.ylabel('sig.step Output')

```

[language=Python]

## 7 Questions

### 7.1 Question 1